Three-phase power measurement by single-phase power meter



GPM-8310/GPM-8213



Blondel's theorem states that total power is measured with ONE LESS wattmeter than the number of WIRES.

When measuring three-phase power, connect three single-phase power meters to each phase and take the sum of the readings. In general, "The power of a polyphase n-wire circuit can be measured using n-1 single-phase wattmeters regardless of the load balance or unbalance, and is given by the sum of the readings of each wattmeter." According to Brondel's theorem, a three-phase three-wire circuit can be measured with two single-phase wattmeters. This measurement method is called the two wattmeter method.

Three Single-phase Power meter Measurement



Two Single-phase Power meter Measurement



Global Headquarters **GOOD WILL INSTRUMENT CO., LTD.** T +886-2-2268-0389 **F** +886-2-2268-0639

China Subsidiary **GOOD WILL INSTRUMENT (SUZHOU) CO., LTD.** T +86-512-6661-7177 F +86-512-6661-7277

Malaysia Subsidiary GOOD WILL INSTRUMENT (SEA) SDN. BHD. T +604-6111122 F +604-6115225 U.S.A. Subsidiary **INSTEK AMERICA CORP.** T +1-909-399-3535 F +1-909-399-0819 Iapan Subsidiary

TEXIO TECHNOLOGY CORPORATION. T +81-45-620-2305 F +81-45-534-7181 Korea Subsidiary

GOOD WILL INSTRUMENT KOREA CO., LTD. T +82-2-3439-2205 F +82-2-3439-2207

P = P1 + P2= $\dot{U}_{RS} * \dot{I}_{R} + \dot{U}_{TS} * \dot{I}_{T}$ = $(\dot{U}_{R} - \dot{U}_{S})\dot{I}_{R} + (\dot{U}_{T} - \dot{U}_{S})*\dot{I}_{T}$ = $(\dot{U}_{R} * \dot{I}_{R} + \dot{U}_{S}(-\dot{I}_{R} - \dot{I}_{T}) + \dot{U}_{T}*\dot{I}_{T}$ = $\dot{U}_{R} * \dot{I}_{R} + \dot{U}_{S} * \dot{I}_{S} + \dot{U}_{T} * \dot{I}_{T} \therefore (I_{R} + I_{S} + I_{T} = 0)$ = Sum of power for each phase

= Three-phase power



Europe Subsidiary **GOOD WILL INSTRUMENT EURO B.V.** T +31(0)40-2557790 F +31(0)40-2541194

India Subsidiary GW INSTEK INDIA LLP. T +91-80-6811-0600 F +91-80-6811-0626





Website Fa

LinkedIn